

Combinational circuits


Binary Adder

Table 4-3
Half Adder


x	y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$S = x'y + xy'$$

$$C = xy$$

 
 
$$(a) \begin{aligned} S &= xy' + x'y \\ C &= xy \end{aligned}$$



$$(b) \begin{aligned} S &= x \oplus y \\ C &= xy \end{aligned}$$

Fig. 4-5 Implementation of Half-Adder


Binary Adder

Table 4-4
Full Adder


<i>x</i>	<i>y</i>	<i>z</i>	<i>C</i>	<i>S</i>
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = x'y'z + x'yz' + xy'z' + xyz$$

$$C = xy + xz + yz$$

 

$$S = x'y'z + x'yz' + xy'z' + xyz$$

 

$$S = xy + xz + yz$$

$$= xy + xy'z + x'yz$$

Fig. 4-6 Maps for Full Adder

 
 


Fig. 4-7 Implementation of Full Adder in Sum of Products


Binary Adder

Table 4-4
Full Adder


x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = x'y'z + x'yz' + xy'z' + xyz$$

$$C = xy'z + x'yz + xy$$

 

$$S = x'y'z + x'yz' + xy'z' + xyz$$

 

$$S = xy + xz + yz$$

$$= xy + xy'z + x'yz$$

Fig. 4-6 Maps for Full Adder

 


Fig. 4-8 Implementation of Full Adder with Two Half Adders and an OR Gate

Parallel Adder

Ripple Carry Adder

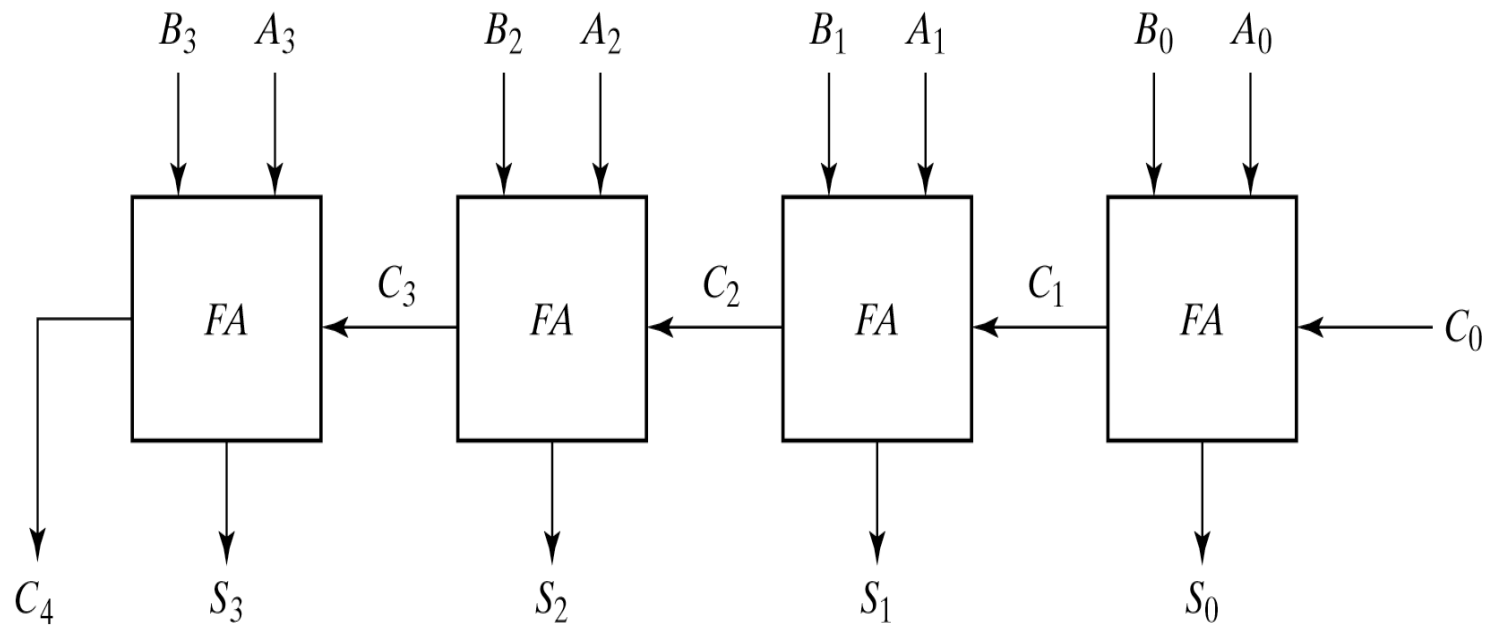


Fig. 4-9 4-Bit Adder

Carry Look-ahead Generator

 


Fig. 4-11 Logic Diagram of Carry Lookahead Generator

Magnitude comparator

 


Fig. 4-17 4-Bit Magnitude Comparator

Decoders

- The decoder is called n-to-m-line decoder, where $m \leq 2^n$.
- the decoder is also used in conjunction with other code converters such as a BCD-to-seven-segment decoder.
- 3-to-8 line decoder: For each possible input combination, there are seven outputs that are equal to 0 and only one that is equal to 1.

Implementation and truth table

Table 4-6

Truth Table of a 3-to-8-Line Decoder

Inputs			Outputs							
x	y	z	D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

 


Fig. 4-18 3-to-8-Line Decoder

Encoder

Table 4-7
Truth Table of Octal-to-Binary Encoder


Inputs								Outputs		
D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	x	y	z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

$$z = D_1 + D_3 + D_5 + D_7$$

$$y = D_2 + D_3 + D_6 + D_7$$


$$x = D_4 + D_5 + D_6 + D_7$$

Multiplexer and Demultiplexer

 

Decoder with enable input

 A demultiplexer is a circuit that receives information on a single line and transmits this information on one of 2^n possible output lines.



(a) Logic diagram

E	A	B	D_0	D_1	D_2	D_3
1	X	X	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

(b) Truth table

Fig. 4-19 2-to-4-Line Decoder with Enable Input

Multiplexers


$S = 0, Y = I_0$

$S = 1, Y = I_1$


Truth Table →

S	Y
0	I_0
1	I_1

$$Y = S'I_0 + SI_1$$

 


(a) Logic diagram

 

(b) Block diagram

Fig. 4-24 2-to-1-Line Multiplexer

Constructing larger decoders

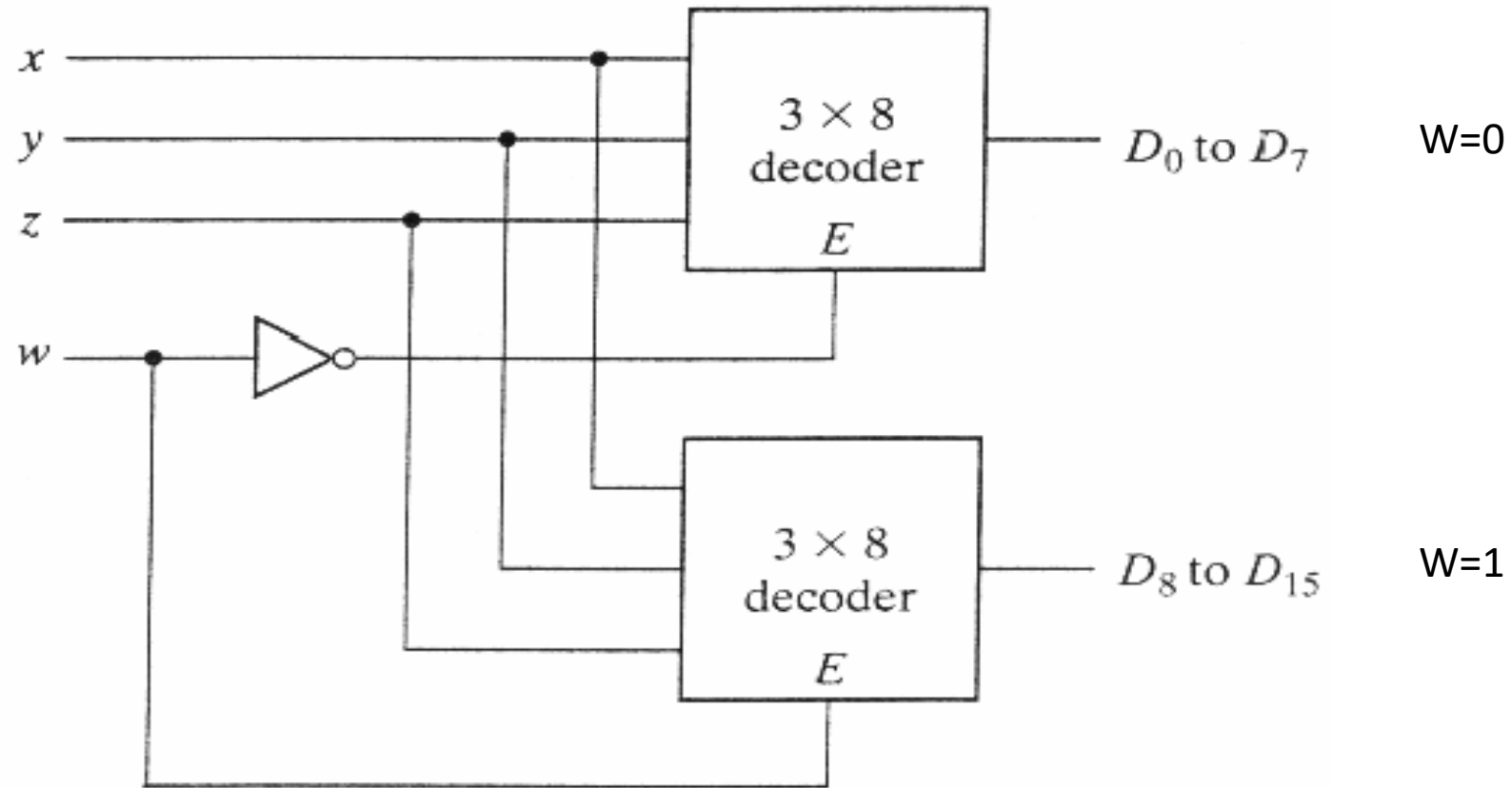


Implementing combinational logic functions using decoders

Truth Table for 1-bit Binary Adder

X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S(X,Y,Z) = \sum m(1,2,4,7)$$

$$C(X,Y,Z) = \sum m(3,5,6,7)$$

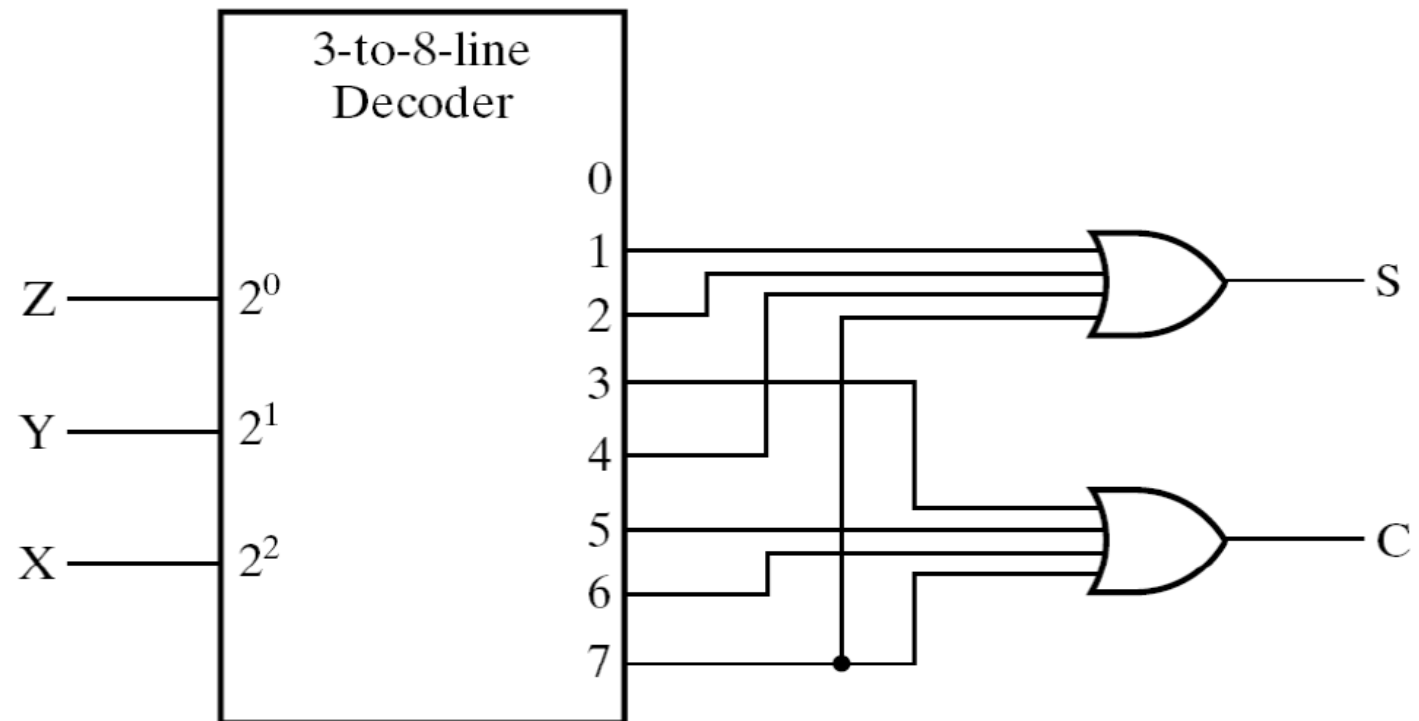


Implementing combinational logic functions using decoders

$$F_1 = x'y'z' + xz = \Sigma(0,5,7)$$

$$F_2 = xy'z' + x'y = \Sigma(2,3,4)$$

$$F_3 = x'y'z + xy = \Sigma(1,6,7)$$

 


Implementing combinational logic functions using decoders

$$F_1 = (y' + x)z$$



$$F_2 = y'z' + xy' + yz'$$

$$F_3 = (x' + y)z$$


4 to 1 multiplexer

 

4 to 1 multiplexer

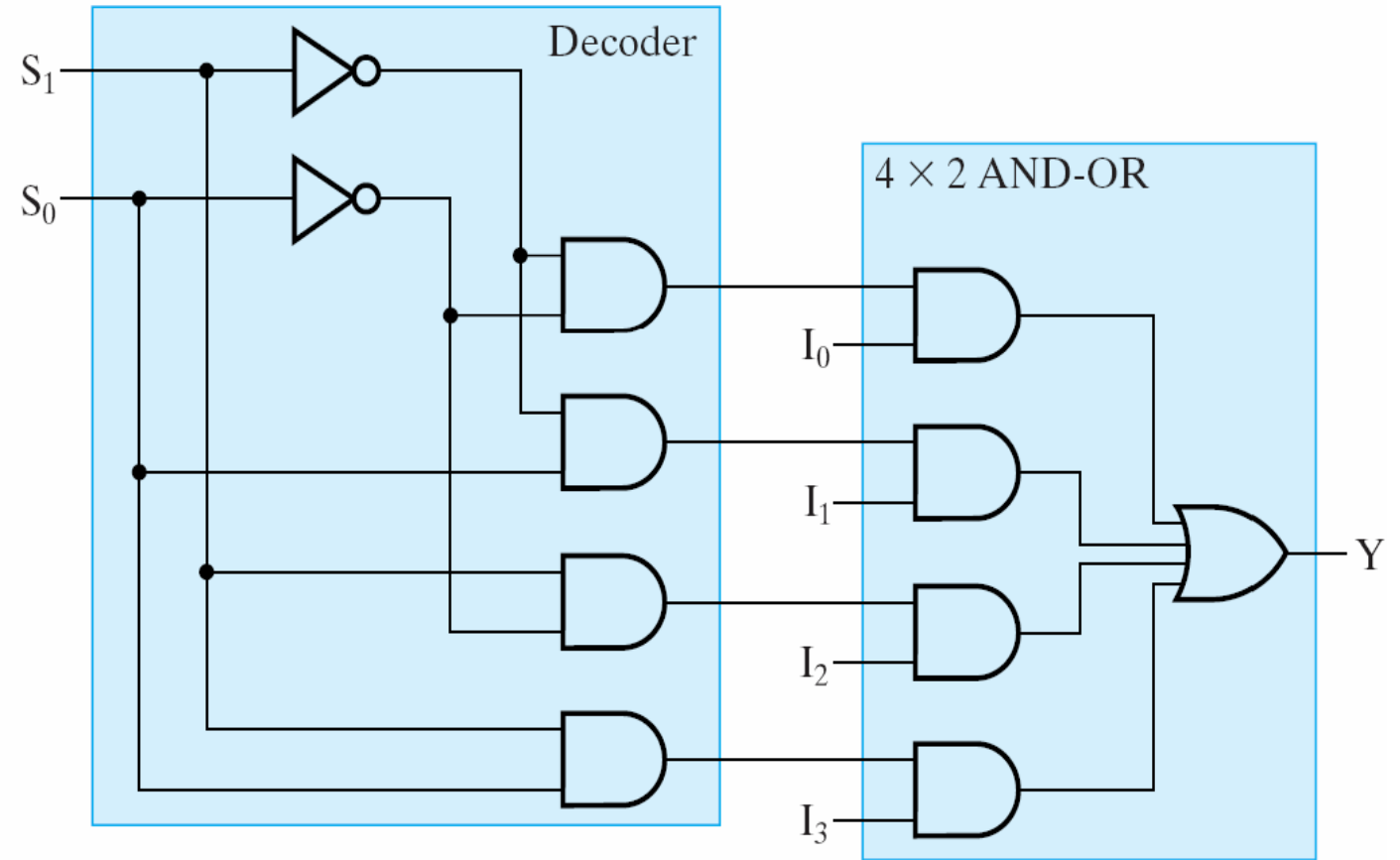 

Construction of larger multiplexers

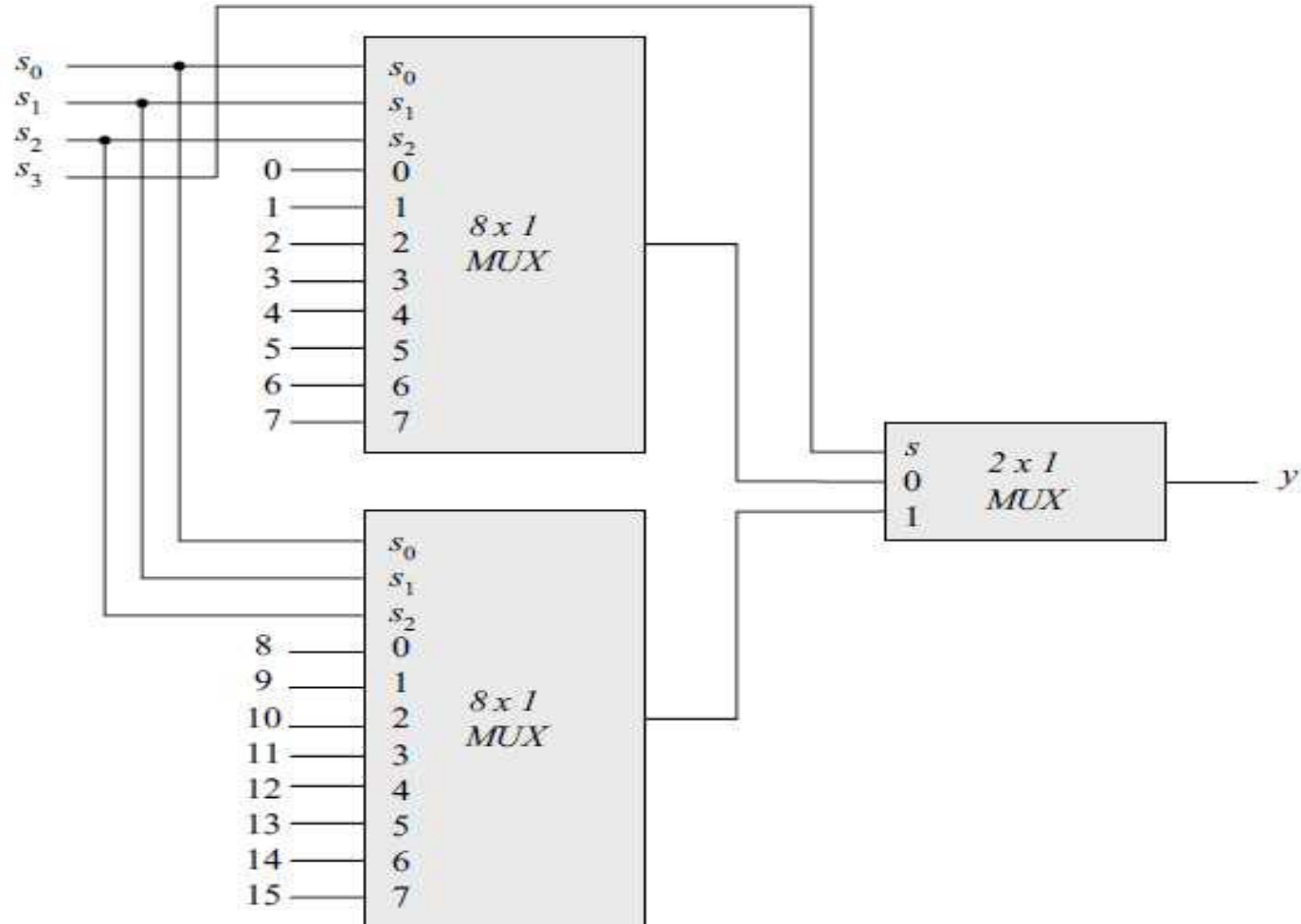



MUX implementation of a binary adder bit

Truth Table for 1-bit Binary Adder

X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S(X,Y,Z) = \sum m(1,2,4,7)$$


$$C(X,Y,Z) = \sum m(3,5,6,7)$$

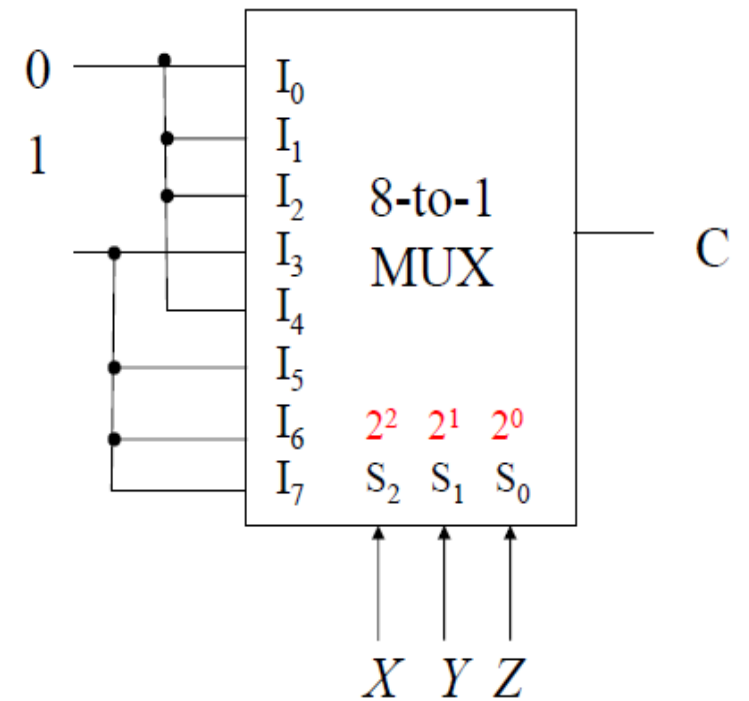 


Implementing combinational logic functions using multiplexer

$$F(A,B,C,D) = \Sigma(1,3,4,11,12,13,14,15)$$

A	B	C	D	F	
0	0	0	0	0	F = D
0	0	0	1	1	
0	0	1	0	0	F = D
0	0	1	1	1	
0	1	0	0	1	F = \overline{D}
0	1	0	1	0	
0	1	1	0	0	F = 0
0	1	1	1	0	
1	0	0	0	0	F = 0
1	0	0	1	0	
1	0	1	0	0	F = D
1	0	1	1	1	
1	1	0	0	1	F = 1
1	1	0	1	1	
1	1	1	0	1	F = 1
1	1	1	1	1	

 

4-bit Adder-Subtractor

 

Priority Encoder

