

B. E. Computer Science and Engineering Second Year First Semester Exam – 2022**DIGITAL LOGIC AND CIRCUITS****Time: 3 Hrs.****Full Marks: 70****Answer all parts of a question in contiguous locations.**

1. [CO3] Characteristic equation of J-K flip-flop is: 2
 - a) $Q(t+1) = Q'(t) \cdot J + Q(t) \cdot K'$
 - b) $Q(t+1) = Q(t) \cdot J' + Q'(t) \cdot K'$
 - c) $Q(t+1) = Q(t) \cdot J + Q'(t) \cdot K'$
 - d) $Q(t+1) = Q(t) \cdot J' + Q'(t) \cdot K$

2. [CO3] Tick the correct statement(s): 2
 - a) Serial adders are slow, requires less hardware and the carry propagation time is fixed.
 - b) Serial adders are slow, requires less hardware but the carry propagation time varies.
 - c) Parallel adders are fast, requires more hardware but the carry propagation time varies.
 - d) None of the above statements is true

3. [CO5] A 4-bit A / D converter implemented with parallel comparators require 2
 - a) 4 nos. of comparators and 4 nos. of D flip-flops
 - b) 8 nos. of comparators and 8 nos. of D flip-flops
 - c) 12 nos. of comparators and 12 nos. of D flip-flops
 - d) 16 nos. of comparators and 16 nos. of D flip-flops

4. [CO5] Tick the correct statement(s): 2
 - a) Weighted register type DAC is more accurate than R-2R Ladder DAC
 - b) R-2R Ladder DAC is more accurate than Weighted register type DAC
 - c) Both of them have the same accuracy.
 - d) R-2R Ladder DAC can be easily fabricated as an IC chip

5. [CO4] Tick the correct statement(s): 2
 - a) Resistor Transistor Logic (RTL) suffers from current hogging.
 - b) For RTL fan-in and fan-out is limited
 - c) For RTL propagation delay is a function fan-in and fan-out.
 - d) Diode Transistor Logic (DTL) has lesser number of fan-in and fan-out.

6. [CO4] For 555 timer, tick the correct statement(s): 2
- a) Two comparator circuits control its function.
 - b) In astable mode, duty cycle of the waveform is controlled by one external capacitor and one external resistor.
 - c) monostable mode, timing is controlled by one external capacitor and one external resistor.
 - d) The output buffer contains a high value capacitor.
7. [CO3] The output of the right-most flip-flop of a 4-bit ring counter is used as the clock input to a 4-bit switch tail ring counter. If the frequency of the clock input is 160 Hz, what will be frequency of the output of the right-most flip-flop of the switch tail ring counter? 2
- a) 640 Hz
 - b) 40 Hz
 - c) 320 Hz
 - d) 5 Hz
8. [CO3] A 4-to-1 MUX realizes a 3-variable function $f(x,y,z) = xy+xz'$, which of the following is correct? 2
- a) $I_0 = x, I_1 = 0, I_2 = y, I_3 = z$
 - b) $I_0 = x, I_1 = 0, I_2 = y, I_3 = z$
 - c) $I_0 = x, I_1 = 0, I_2 = y, I_3 = z$
 - d) $I_0 = x, I_1 = 0, I_2 = y, I_3 = z$
9. [CO1] Let a receiver receives a Hamming coded bit pattern 0011011. It is checked for any possible error during transmission. 2
- a) Received bit pattern is correct.
 - b) Error occurred at the 6th bit position and correct one is 0011001
 - c) Error occurred at the 3rd bit position and correct one is 0001011
 - d) Error occurred at the 4th bit position and correct one is 0010011
10. [CO2] Let $f(A,B,C,D) = A \oplus B \oplus C \oplus D$, then which one of the following is correct? 2
- a) $f(A,B,C,D) = \sum(1,2,6,8, 10, 12,13,14)$
 - b) $f(A,B,C,D) = \sum(1,2,4,7, 8,11,13,14)$
 - c) $f(A,B,C,D) = \sum(2,4,5,6, 12,13,14,15)$
 - d) $f(A,B,C,D) = \sum(2,4,5,6, 12,13,14,15)$
11. [CO1] Let $f(A,B,C) = ((A(AB)')' (B(AB)')')'$, then which one of the following is correct? 2
- a) $f(A,B,C) = ((A' + AB) (B' + A'B'))'$
 - b) $f(A,B,C) = ((A + B)' + (A' + B'))'$
 - c) $f(A,B,C) = ((A' + A'B') (B' + AB))'$
 - d) $f(A,B,C) = ((A + AB) (B' + A'B'))'$

12. [CO3] A sequential circuit has two pulse inputs x_1 and x_2 . The output of the circuit z becomes 1 when one or more x_1 pulses are followed by two x_2 pulses. The output then remains 1 for all subsequent x_2 pulses until an x_1 pulse occurs. 12
- Draw the state diagram and corresponding minimal state table.
 - Synthesize the circuit using R-S flip-flops.
13. [CO3] Given the following flow table of an asynchronous circuit. 12
- | y_1y_2 | Y_1Y_2 | | | |
|----------|----------|----|----|----|
| | x_1x_2 | | | |
| | 00 | 01 | 11 | 10 |
| 00 | 00 | 11 | 00 | 11 |
| 01 | 11 | 01 | 11 | 11 |
| 11 | 11 | 11 | 00 | 11 |
| 10 | 00 | 10 | 11 | 11 |
- Mark all the stable states.
 - Find all the races and indicate which of them are critical and which are not.
 - Is there any infinite race cycle?
 - Suggest a new set of state assignment so that the new flow table contains no critical races.
14. [CO2] Minimize the following Boolean function using Quine – McCluskey. 12
- $F(A, B, C, D, E) = \sum (0,4,6,11,13,15,21,25,29) + d (2,9,17,27,31)$
- Show all steps clearly.
15. [CO3] Design a BCD to Excess – 3 encoder using multiplexers. Specify the type of multiplexers and number of such multiplexers to be used in the design. 12
-