
 


Sequential Circuit Design

 3-bit asynchronous (ripple) binary counter




(a)




(b)


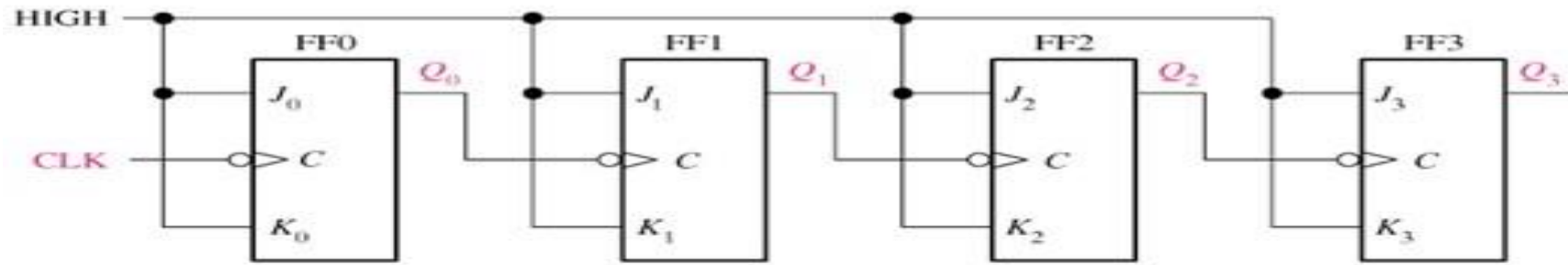
4-bit asynchronous (ripple) binary counter (negative edge triggered)





(a)

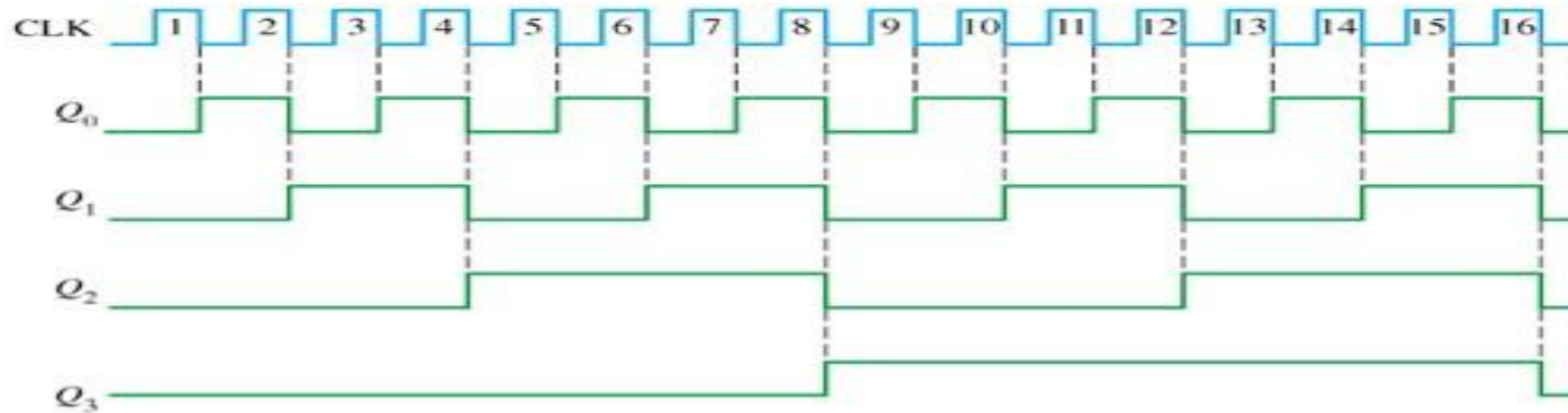

2-bit synchronous binary counter

 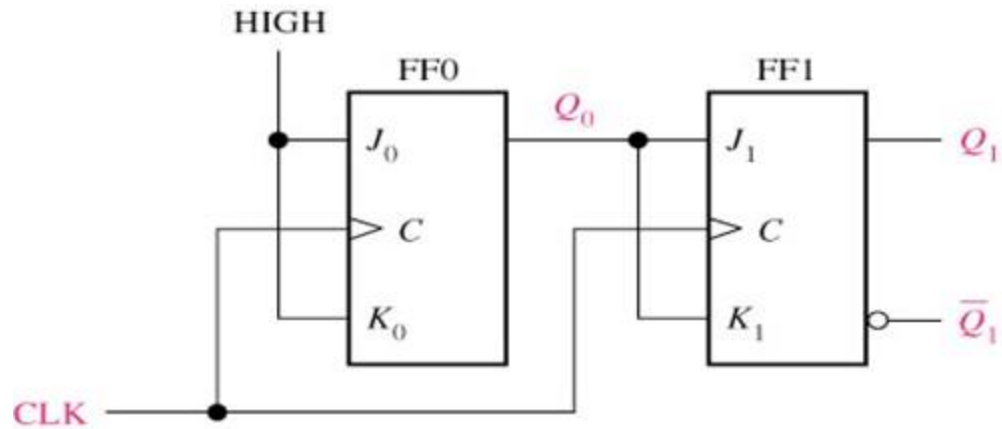

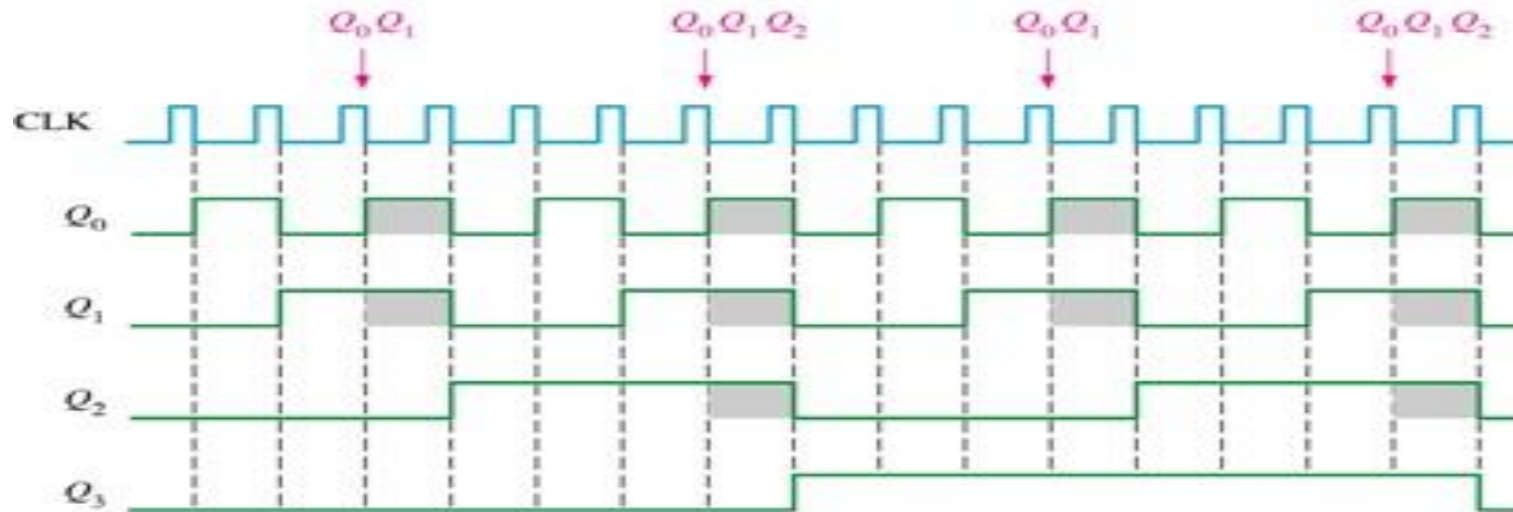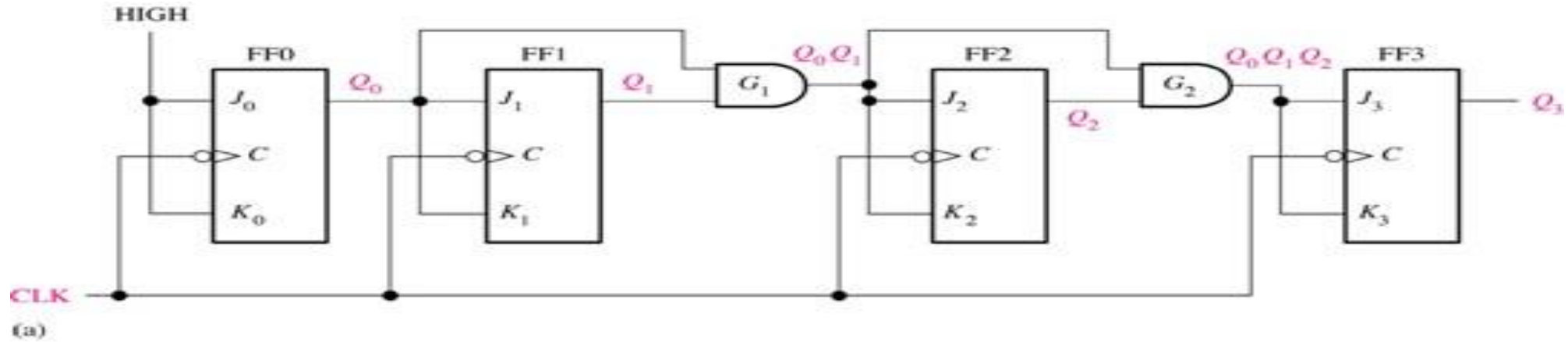4-bit synchronous binary counter (negative edge triggered)




- The number of flip-flops determines the count limit or number of states.


$$(\text{STATES} = 2^{\text{\# of flip flops}})$$

- Number of states used is called the MODULUS
- A Modulus-12 counter would count from 0 (0000) to 11 (1011) and requires four flip-flops (16 states - 12 used).


Modulo-6 counter (truncated counter)

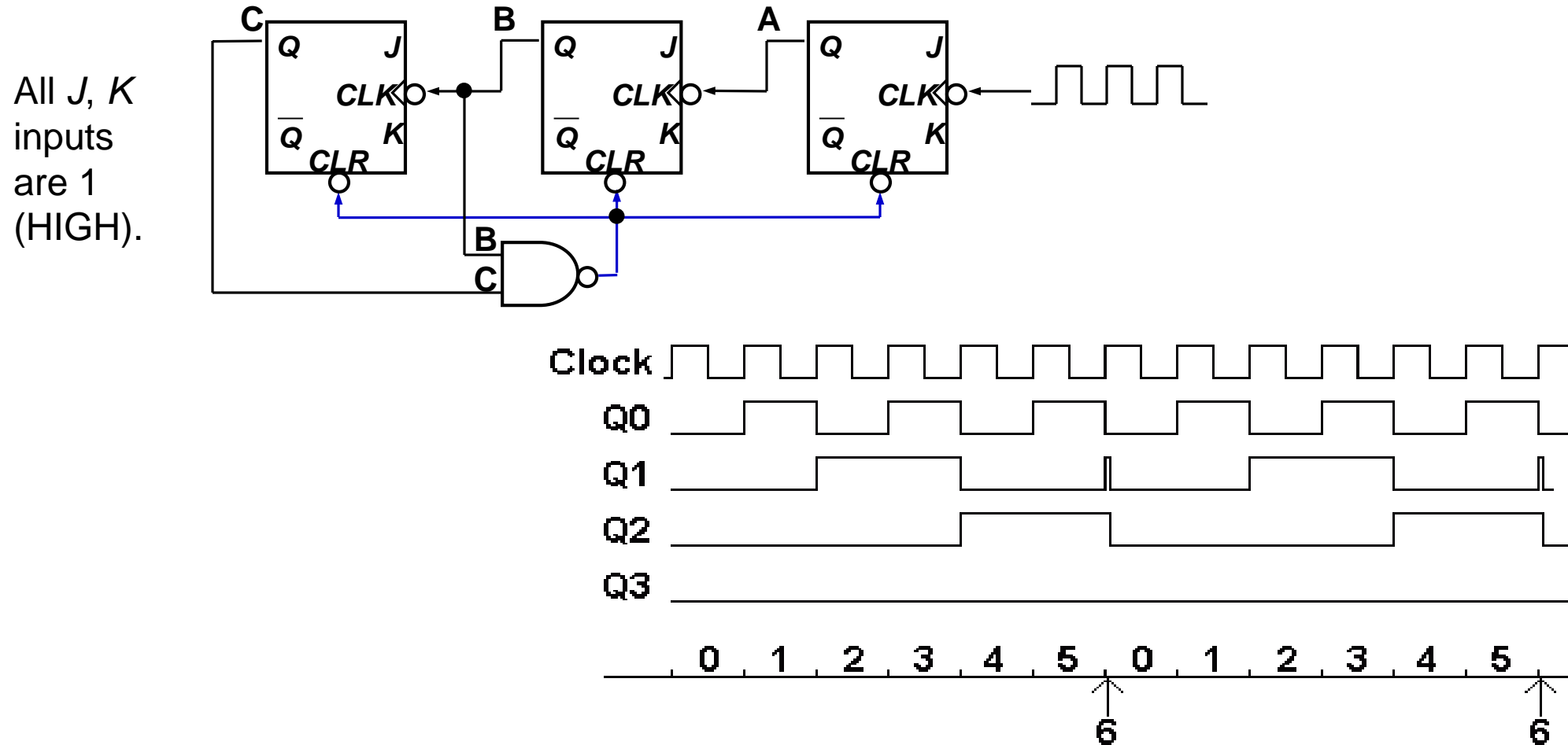


Decade counters (or BCD counters)

 


Up and down counter

 

3-bit binary up counter

 

3-bit binary down counter

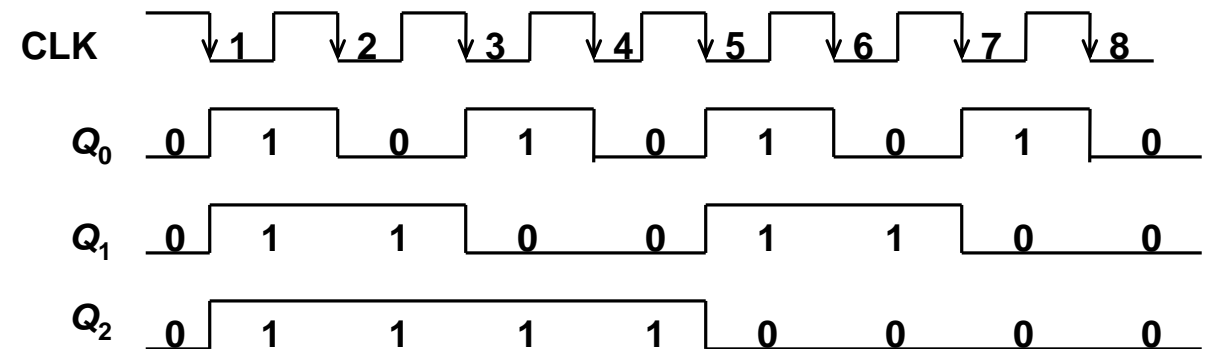


Sequential Circuit Design

- The most general model of a sequential circuit has inputs, outputs, and internal states.
- Mealy model and Moore model
 - They differ in the way the output is generated.
 - In the Mealy model, the output is a function of both the present state and input.
 - Outputs have immediate reaction to inputs
 - As inputs change, so does next state, doesn't commit until clocking event
 - In the Moore model, the output is a function of the present state only.
 - Output does not react immediately to input change

Specifying Outputs for a Moore Machine

Output is only function of state

 - Specify in state bubble in state diagram
- Example: sequence detector for 01 or 10




reset	input	current state	next state	output
1	—	—	A	
0	0	A	B	0
0	1	A	C	0
0	0	B	B	0
0	1	B	D	0
0	0	C	E	0
0	1	C	C	0
0	0	D	E	1
0	1	D	C	1
0	0	E	B	1
0	1	E	D	1

Specifying Outputs for a Mealy Machine


Output is function of state and inputs

 - Specify output on transition arc between states
- Example: sequence detector for 01 or 10



reset	input	current state	next state	output
1	—	—	A	0
0	0	A	B	0
0	1	A	C	0
0	0	B	B	0
0	1	B	C	1
0	0	C	B	1
0	1	C	C	0

Moore FSM General Block Diagram

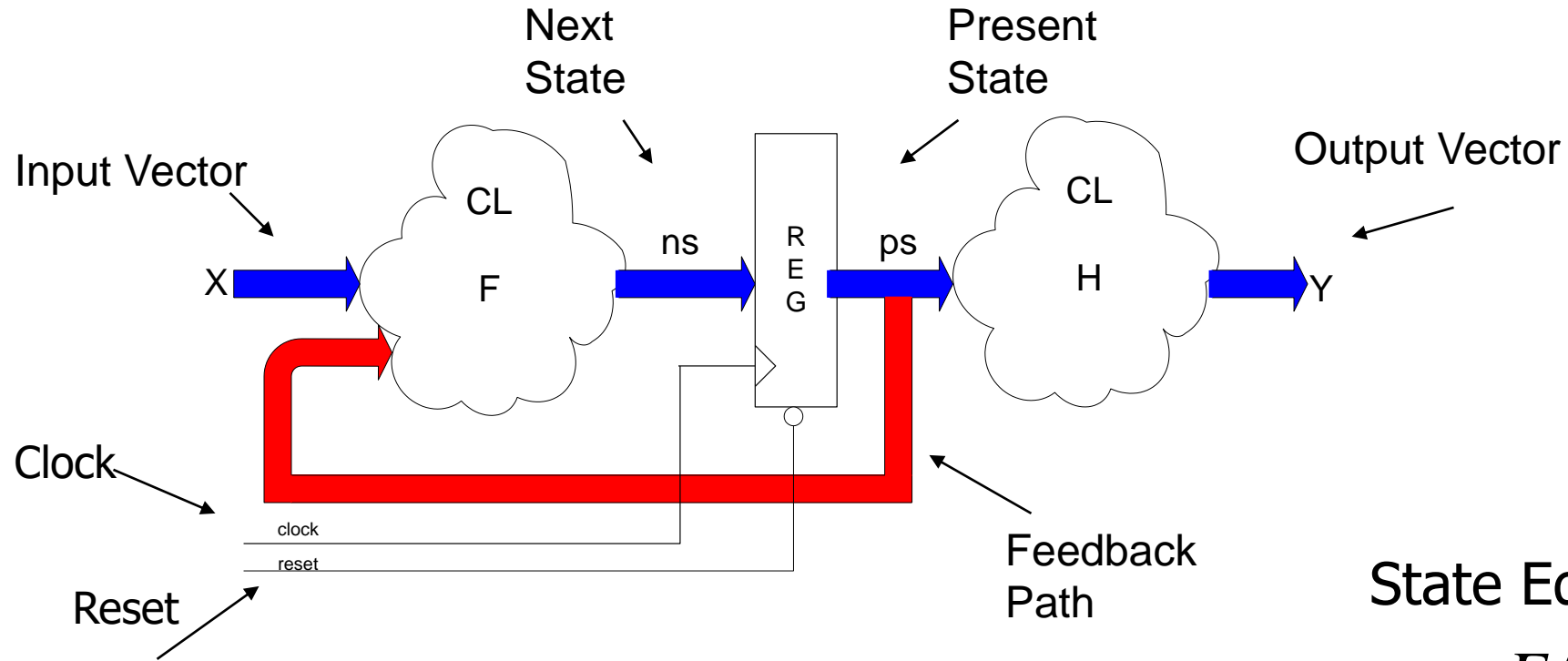

CL= Combinational Logic Cloud


Reg= D Registers

State Equations

$$n_s = F(X, p_s)$$

$$Y = H(p_s)$$

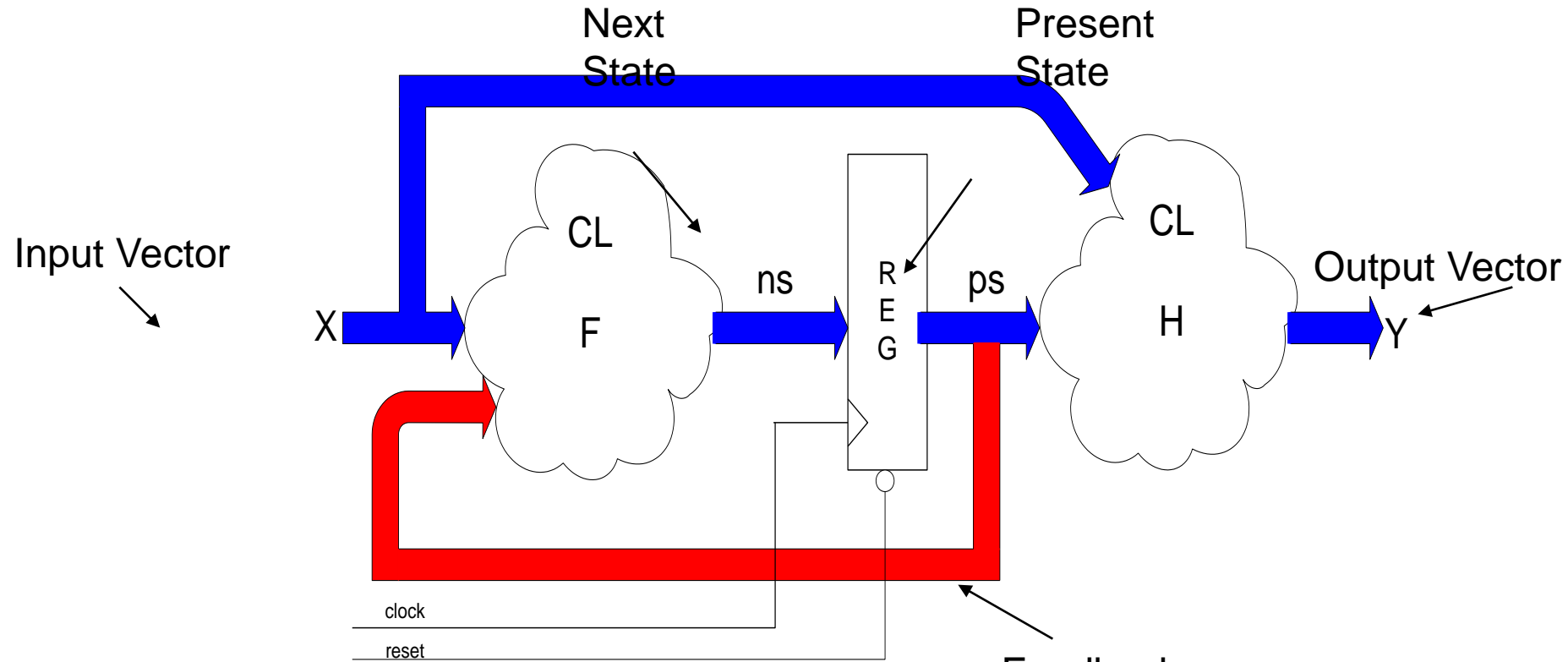Mealy FSM Block Diagram and State Equations



$$n_s = F(X, p_s)$$

$$Y = H(X, p_s)$$

Output Y is also a function of input X

Comparison of Mealy and Moore Machines

- Mealy Machines tend to have less states
 - Different outputs on arcs (n^2) rather than states (n)
- Moore Machines are safer to use
 - Outputs change at clock edge (always one cycle later)
 - In Mealy machines, input change can cause output change as soon as logic is done – a big problem when two machines are interconnected
- Mealy Machines react faster to inputs
 - React in same cycle – don't need to wait for clock
 - In Moore machines, more logic may be necessary to decode state into outputs – more gate delays after