

 
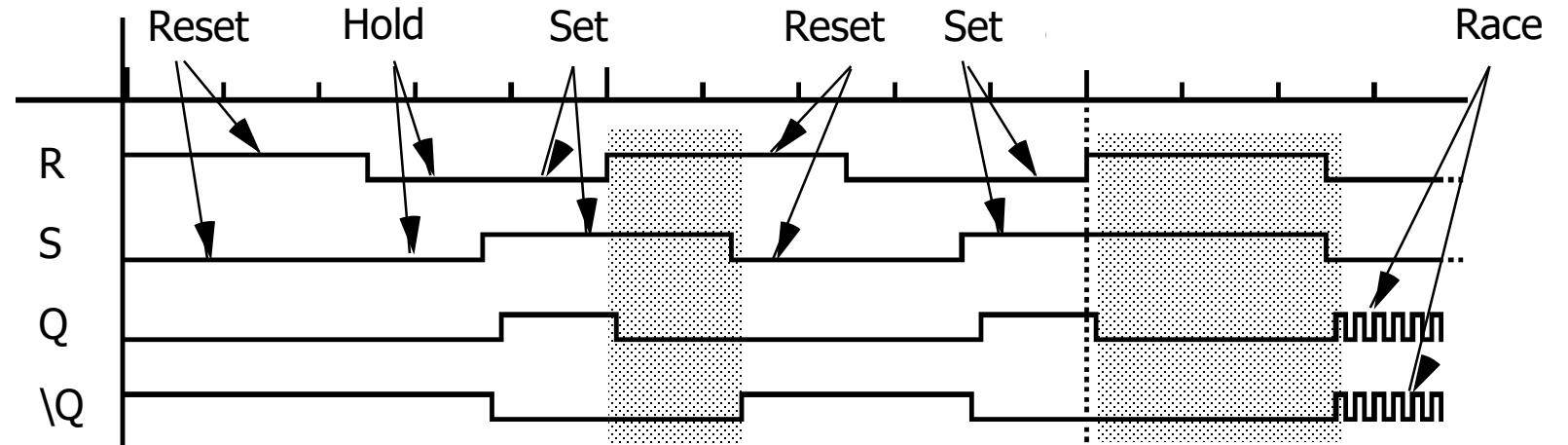




Sequential Circuits

SR Latch


 


 

Gated SR Latch

  


Using clock as gated signal

  


C	S	R	Next state of Q
0	X	X	No change
1	0	0	No change
1	0	1	$Q = 0$; Reset state
1	1	0	$Q = 1$; Set state
1	1	1	Undefined

Clocked SR Latch

 


Q and Q' flip state
when the clock is
high


The D Latch

 


C	D	Next state of Q
0	X	No change
1	0	Q = 0; Reset state
1	1	Q = 1; Set state

 

SR

 


$\overline{S}\overline{R}$

 

D

Fig. 5-7 Graphic Symbols for Latches

 

(a) Graphic Symbol

